

CS2100

COMPUTER ORGANISATION

<http://www.comp.nus.edu.sg/~cs2100/>

## Lecture #12

---

# The Processor: Control



**NUS**  
National University  
of Singapore

School of  
Computing




<https://app.sli.do/event/5P8F43kQW2Vg2Y8TTRVzHu>

# Lecture #12: Processor: Control

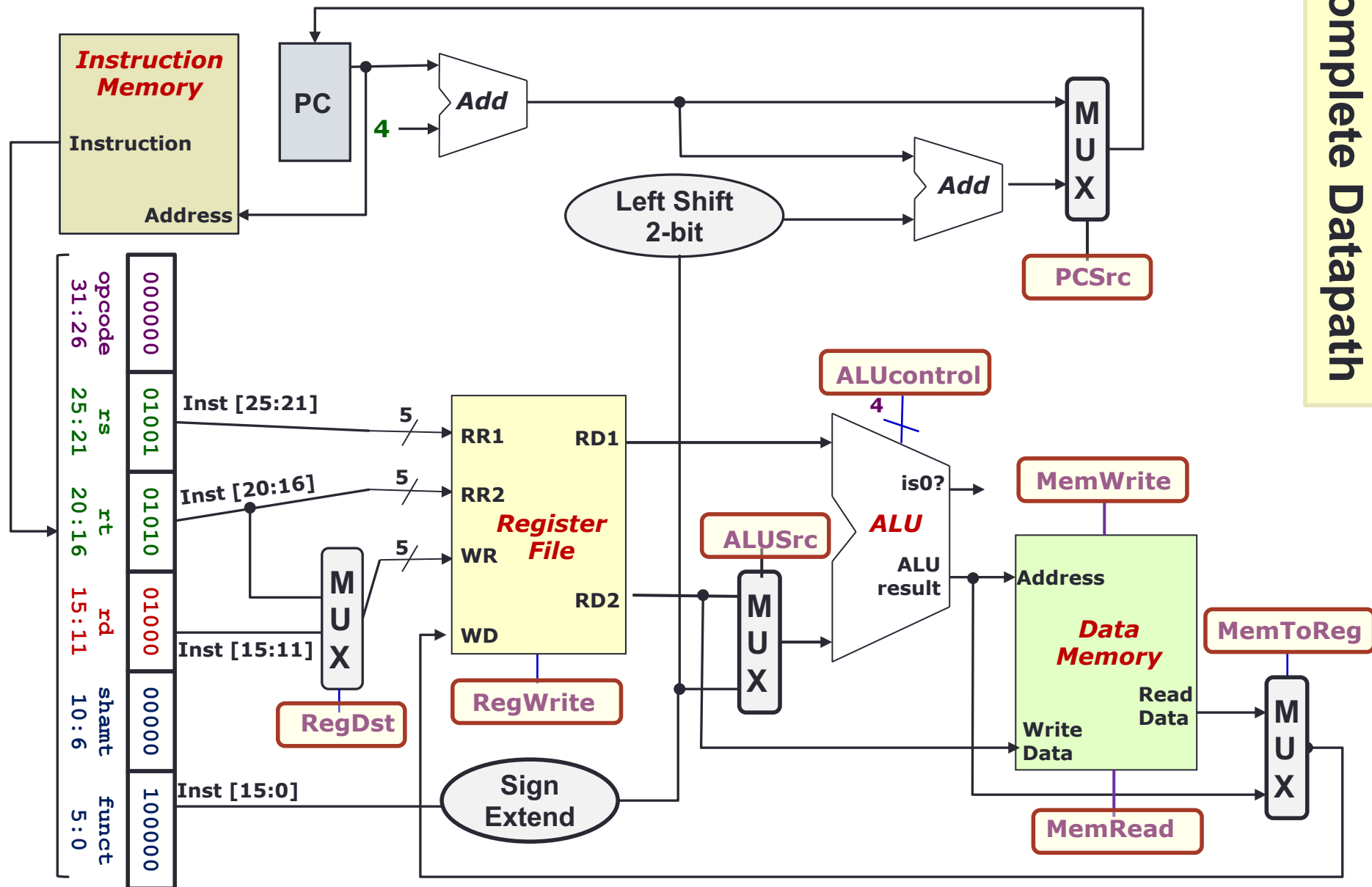1. Identified Control Signals
2. Generating Control Signals: Idea
3. The Control Unit
4. Control Signals
5. ALU Control Signal
6. Instruction Execution






# 1. Identified Control Signals

Control Signal	Execution Stage	Purpose
<b>RegDst</b>	Decode/Operand Fetch	Select the destination register number
<b>RegWrite</b>	Decode/Operand Fetch RegWrite	Enable writing of register
<b>ALUSrc</b>	ALU	Select the 2 <sup>nd</sup> operand for ALU
<b>ALUcontrol</b>	ALU	Select the operation to be performed
<b>MemRead / MemWrite</b>	Memory	Enable reading/writing of data memory
<b>MemToReg</b>	RegWrite	Select the result to be written back to register file
<b>PCSrc</b>	Memory/RegWrite	Select the next PC value
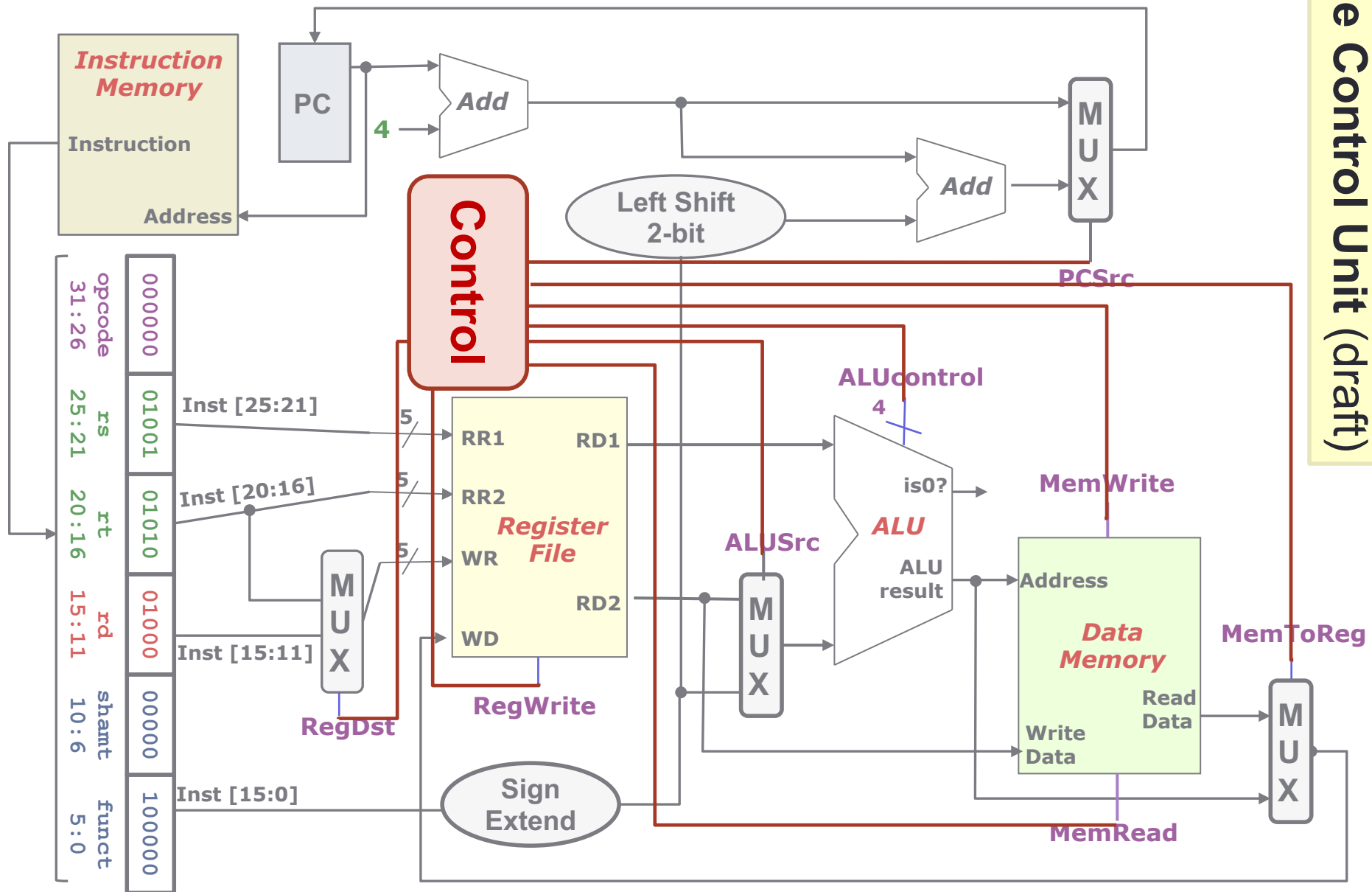
## 2. Generating Control Signals: Idea

- The control signals are generated based on the instruction to be executed:
  - Opcode → Instruction Format
  - Example:
    - R-Format instruction → **RegDst** = 1 (use **Inst**[**15:11**])
    - R-Type instruction has additional information:
      - The 6-bit "**funct**" (function code, **Inst**[**5:0**]) field
- **Idea:**
  - Design a combinational circuit to generate these signals based on Opcode and possibly Function code
    - A **control unit** is needed (a draft design is shown next)






# 3. Let's Implement the Control Unit!

- Approach:
  - Take note of the instruction subset to be implemented:
    - Opcode and Function Code (if applicable)
  - Go through each signal:
    - Observe how the signal is generated based on the instruction opcode and/or function code
  - Construct truth table
  - Design the control unit using logic gates





# 3. MIPS Instruction Subset (Review)

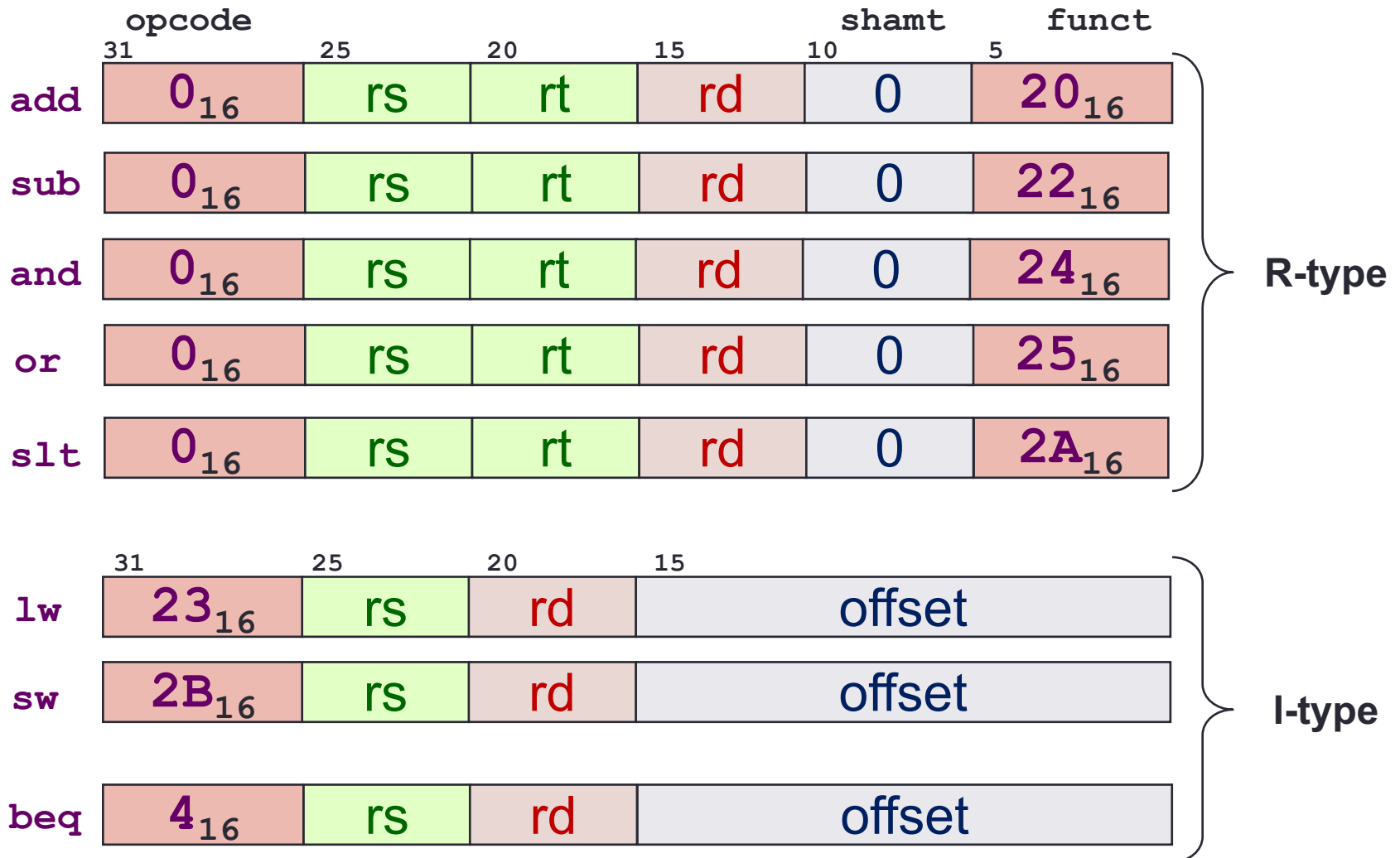



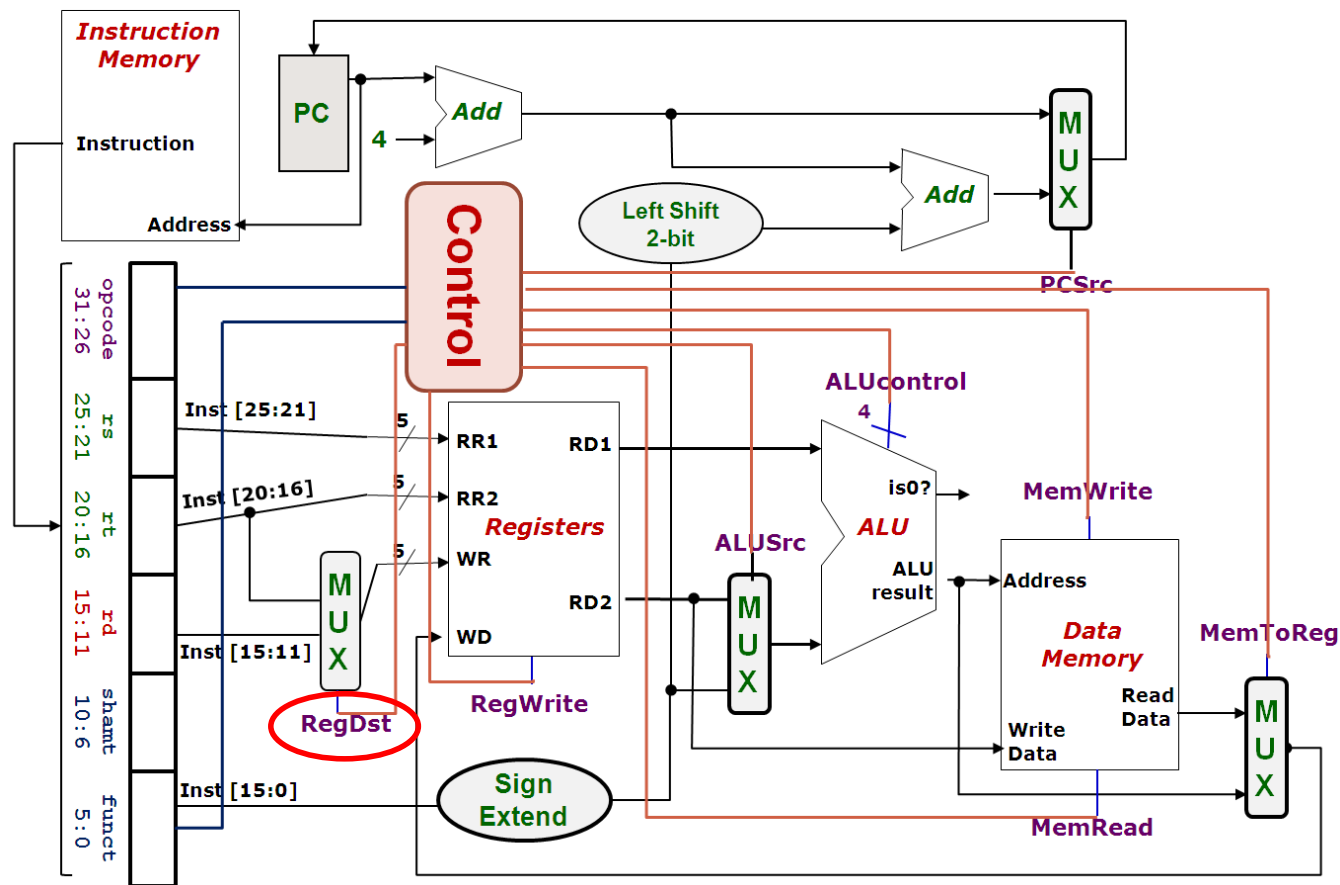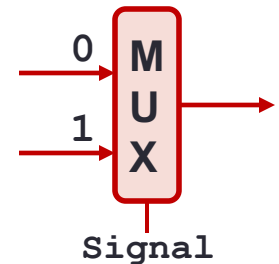
## 4. Control Signal: RegDst

- **False (0):** Write register = **Inst** [20:16]
- **True (1):** Write register = **Inst** [15:11]



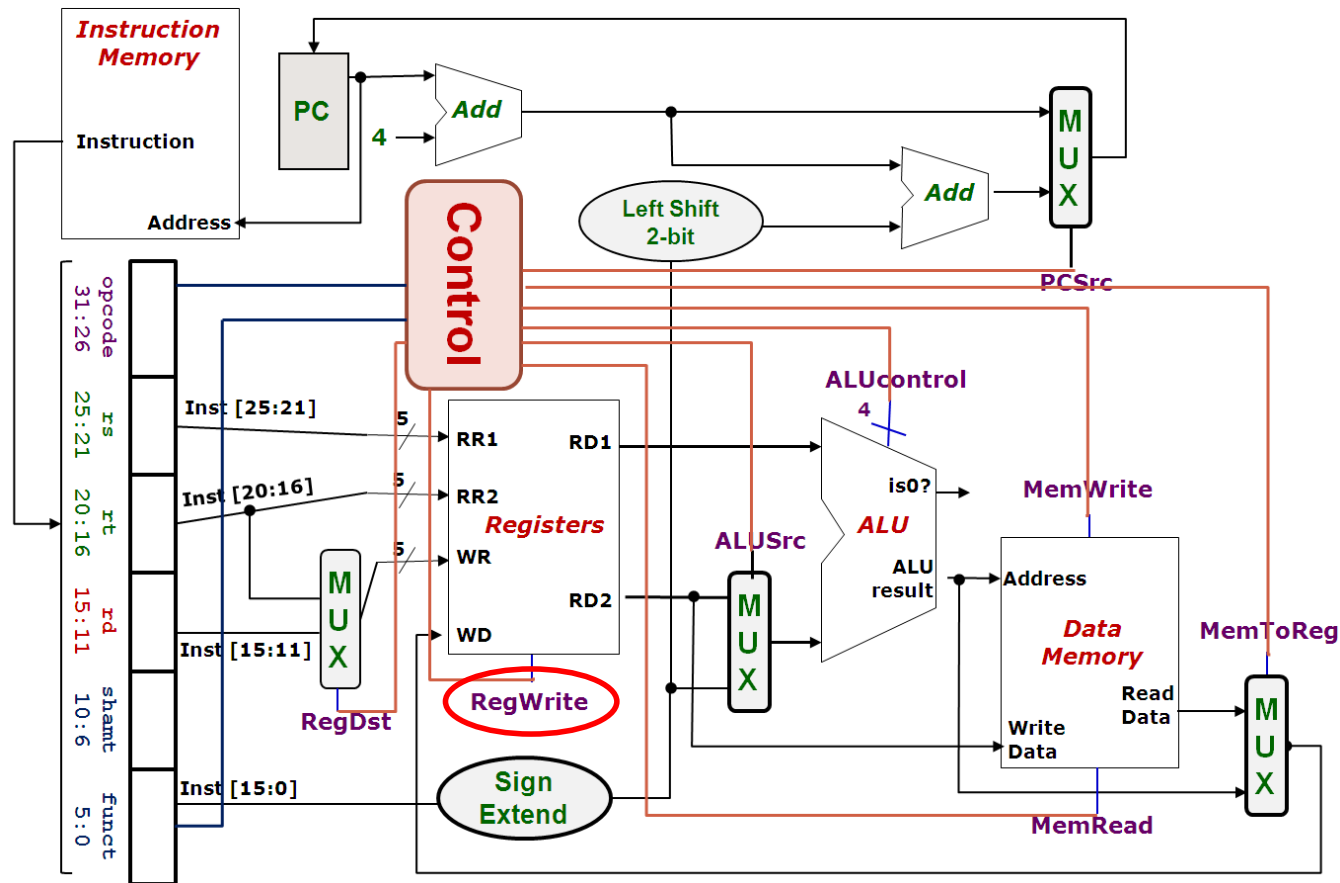
## 4. Control Signal: RegWrite

- **False (0):** No register write
- **True (1):** New value will be written



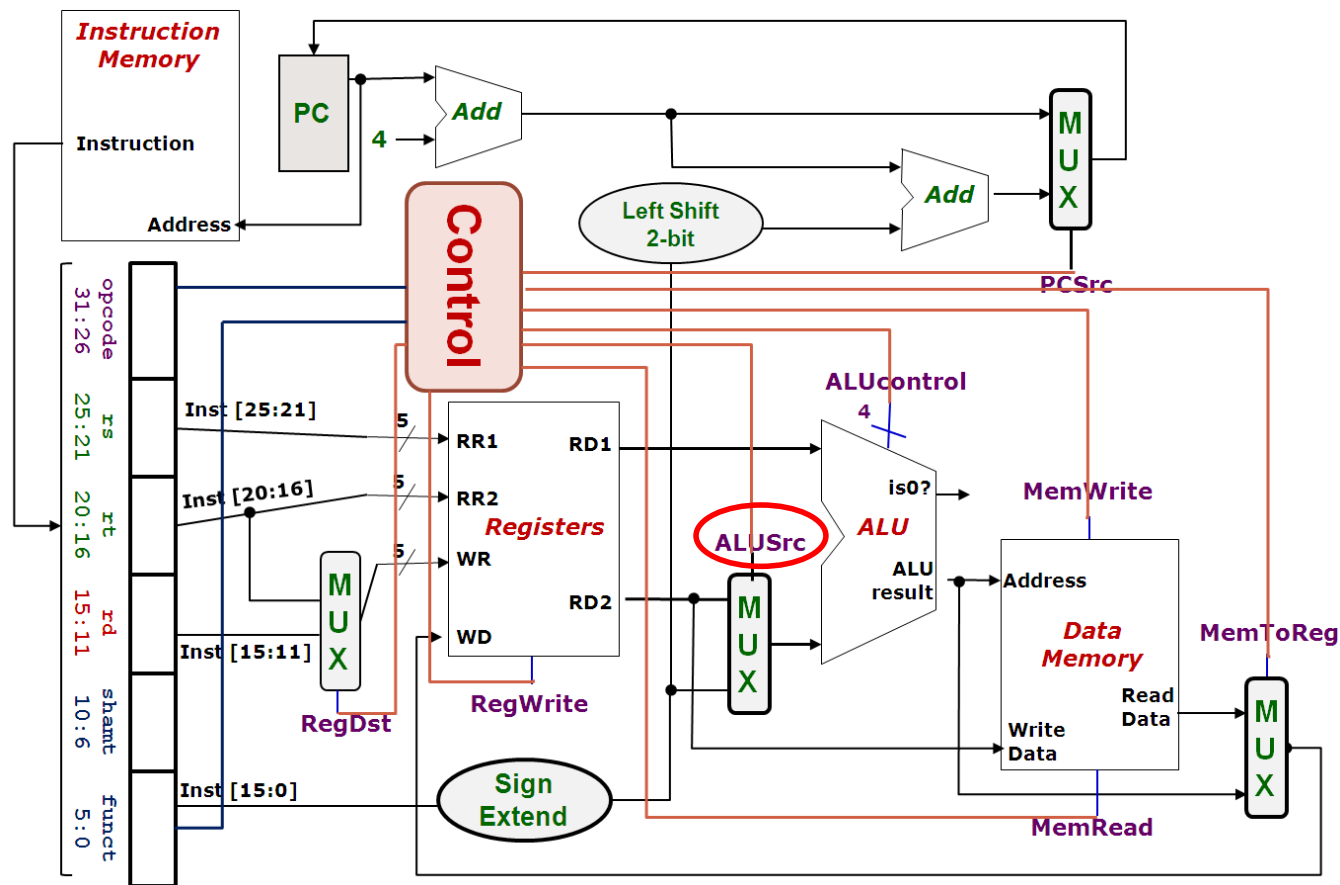
## 4. Control Signal: **ALUSrc**

- **False (0):** Operand2 = Register Read Data 2
- **True (1):** Operand2 = SignExt(**Inst**[15:0])



 
## 4. Control Signal: MemRead

- **False (0):** Not performing memory read access
- **True (1):** Read memory using ***Address***



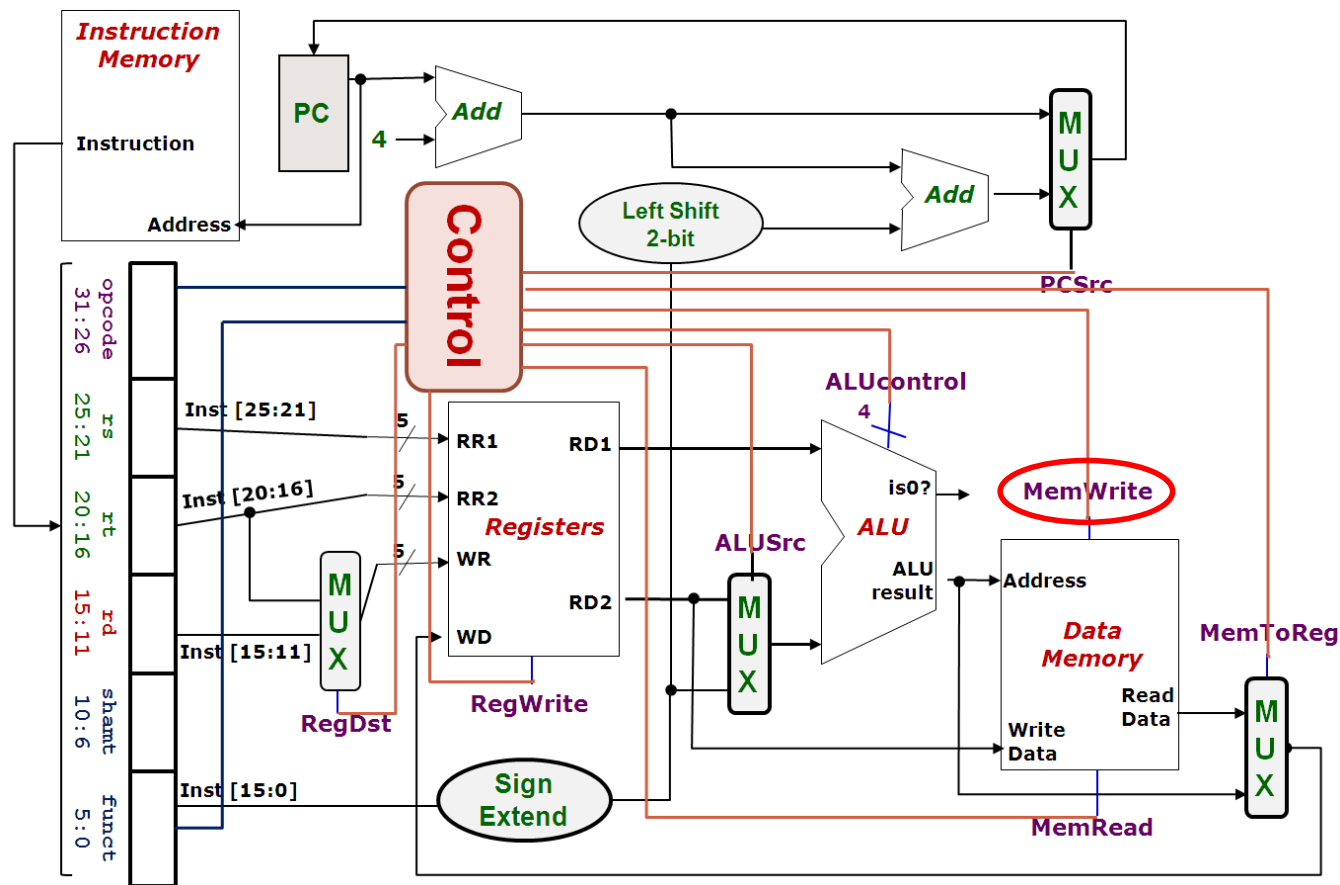
## 4. Control Signal: MemWrite

- **False (0):** Not performing memory write operation
- **True (1):**  $\text{memory}[\text{Address}] \leftarrow \text{Register Read Data 2}$



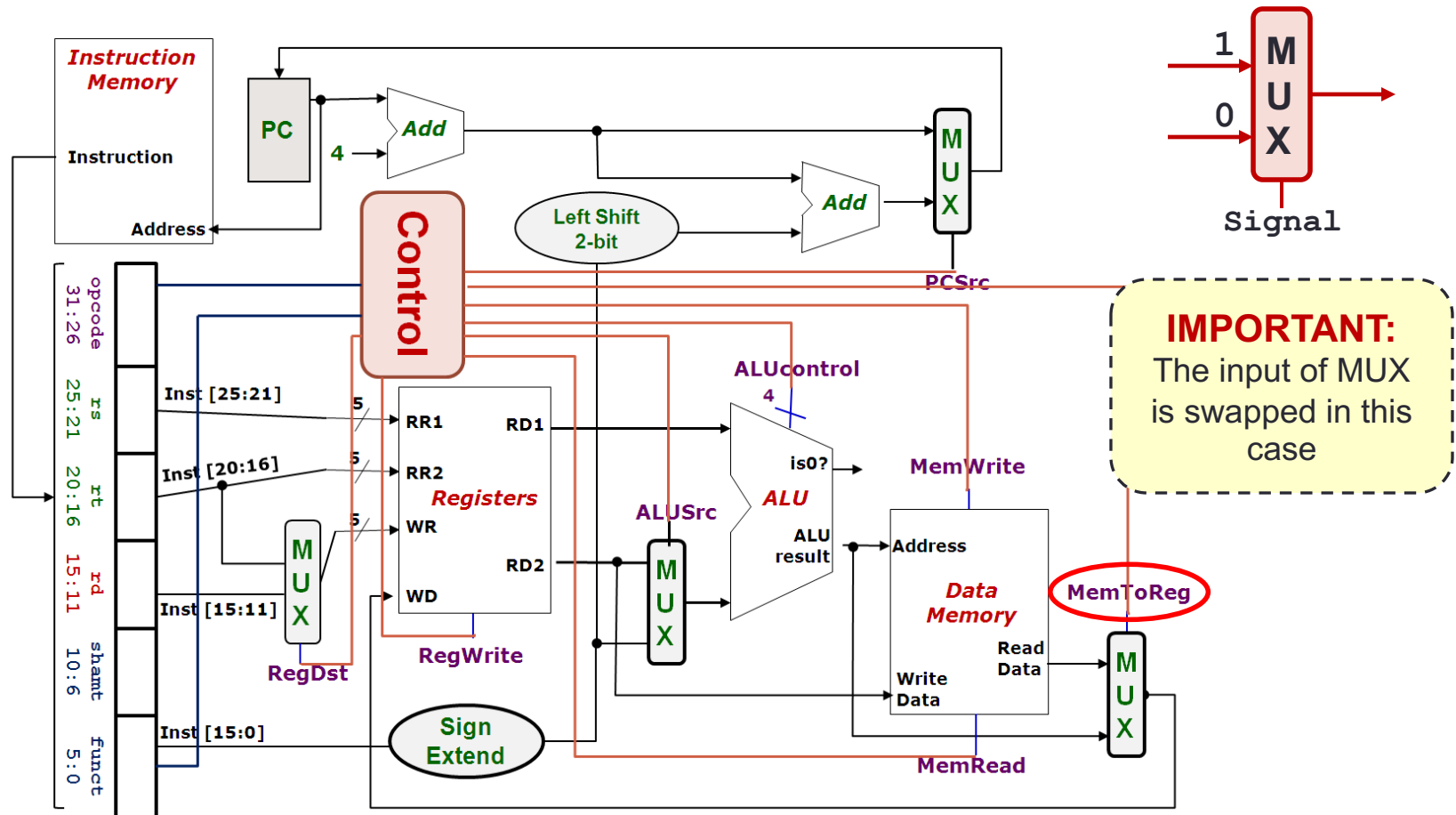
## 4. Control Signal: MemToReg

- **True (1):** Register write data = Memory read data
- **False (0):** Register write data = ALU result



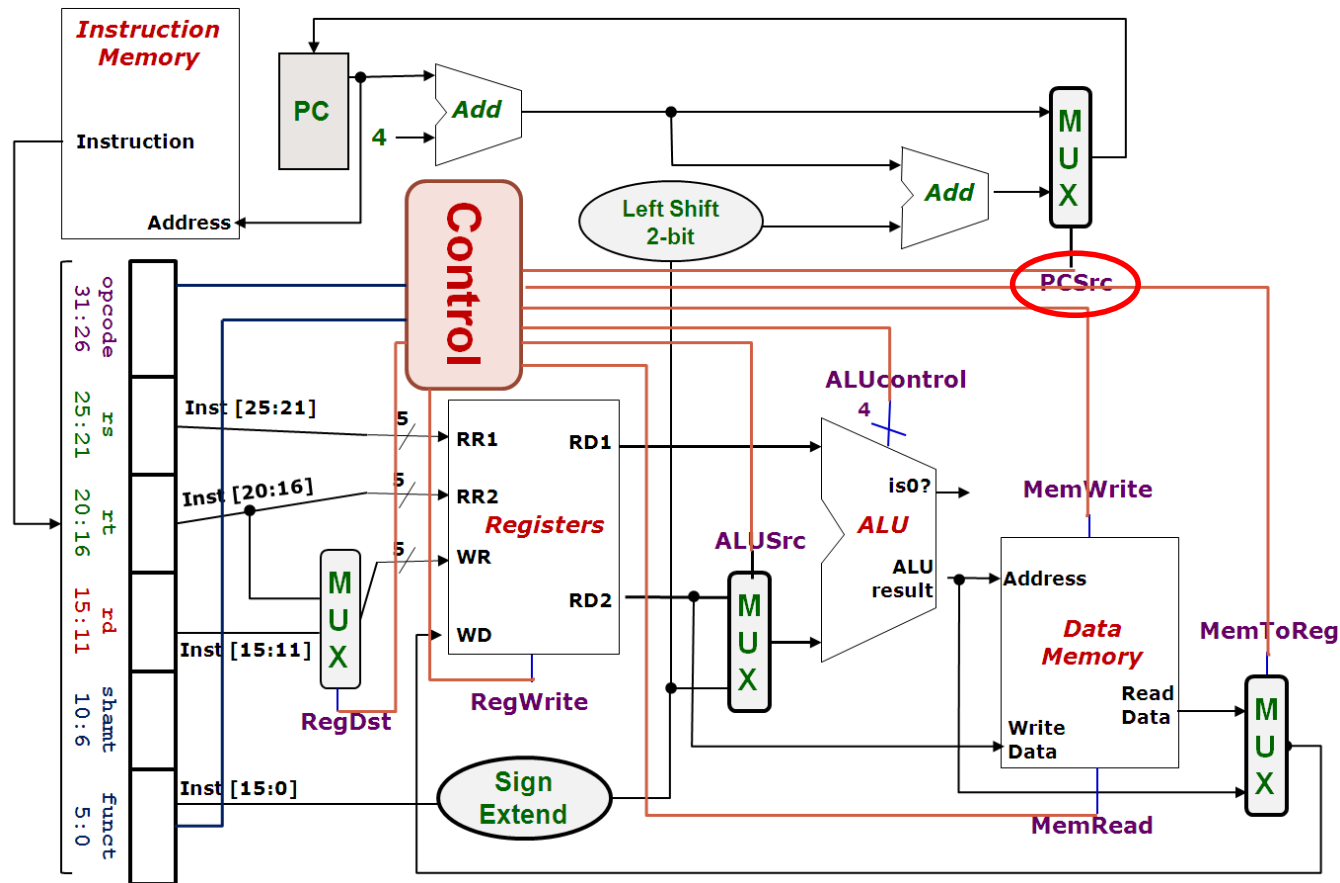
## 4. Control Signal: PCSrc (1/2)

- The "isZero?" signal from the ALU gives us the actual branch outcome (taken/not taken)
- **Idea:** "If instruction is a branch **AND** taken, then..."


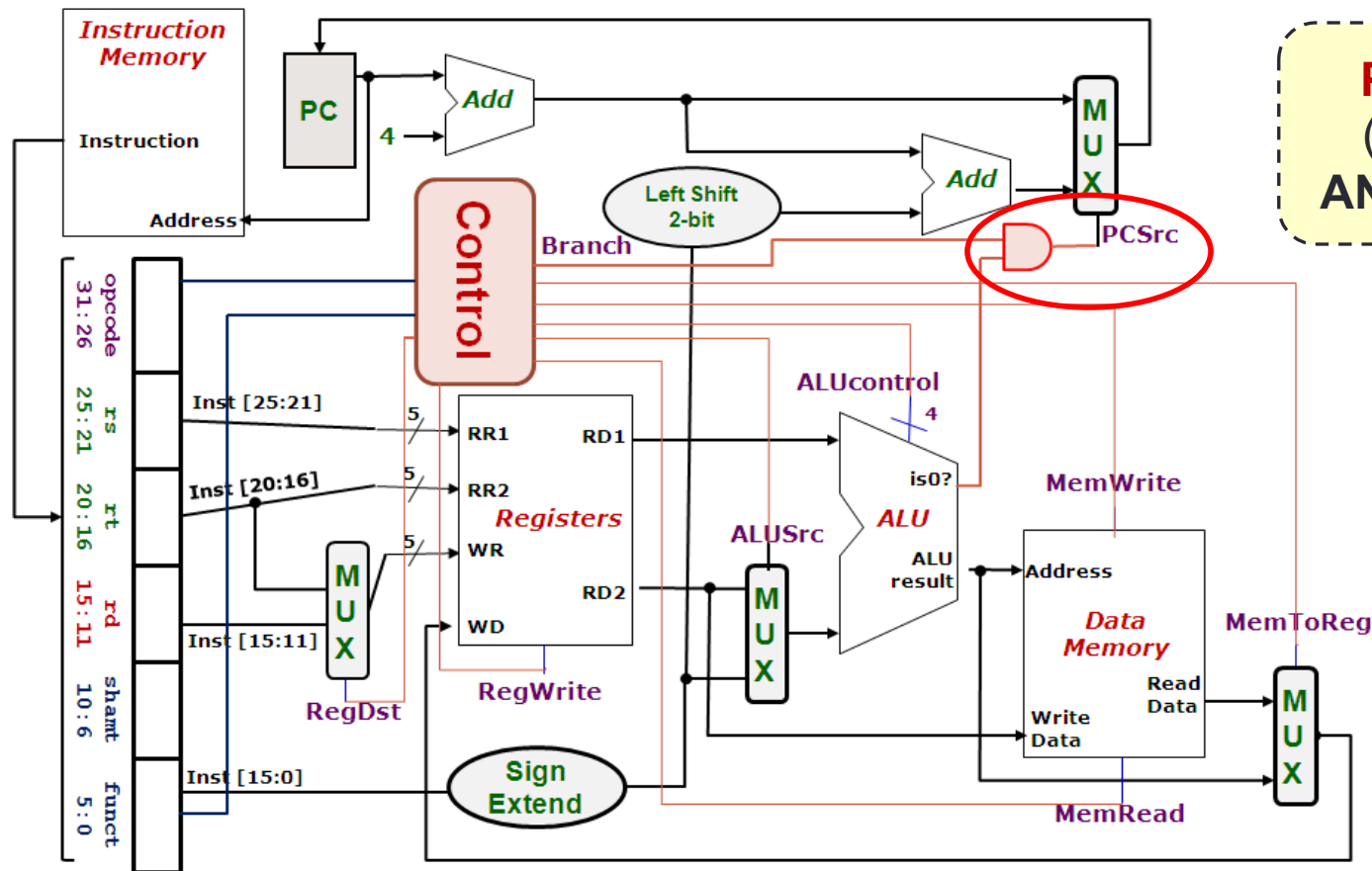
## 4. Control Signal: PCSrc (2/2)

- **False (0):** Next PC = PC + 4
- **True (1):** Next PC = SignExt(**Inst** [15:0]) << 2 + (PC + 4)





## 4. Midpoint Check


- We have gone through almost all of the signals:

- Left with the more challenging **ALUcontrol** signal

Control Signal	Execution Stage	Purpose
RegDst	Decode/Operand Fetch	Select the destination register number
RegWrite	Decode/Operand Fetch RegWrite	Enable writing of register
ALUSrc	ALU	Select the 2 <sup>nd</sup> operand for ALU
ALUcontrol	ALU	Select the operation to be performed
MemRead / MemWrite	Memory	Enable reading/writing of data memory
MemToReg	RegWrite	Select the result to be written back to register file
PCSrc	Memory/RegWrite	Select the next PC value

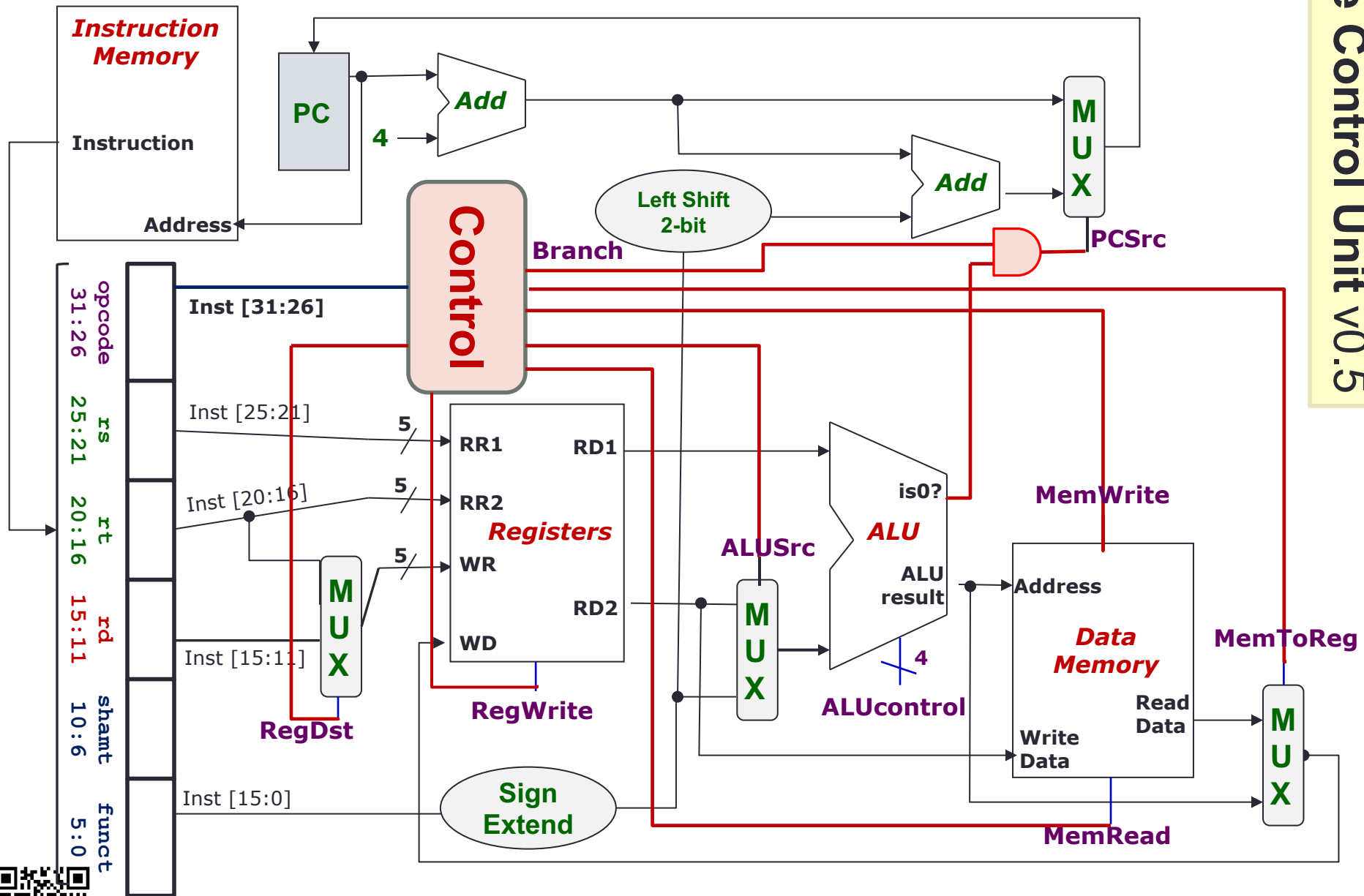- Observation so far:
  - The signals discussed so far can be generated by *opcode* directly
    - Function code is not needed up to this point
- A major part of the controller can be built based on *opcode* alone





## 5. Closer Look at ALU

**Note:** We will cover combinational circuits after the recess.

- The ALU is a combinational circuit:
  - Capable of performing several arithmetic operations
- In Lecture #11:
  - We noted the required operations for the MIPS subset

- Question:
  - How is the **ALUcontrol** signal designed?


ALUcontrol	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	slt
1100	NOR


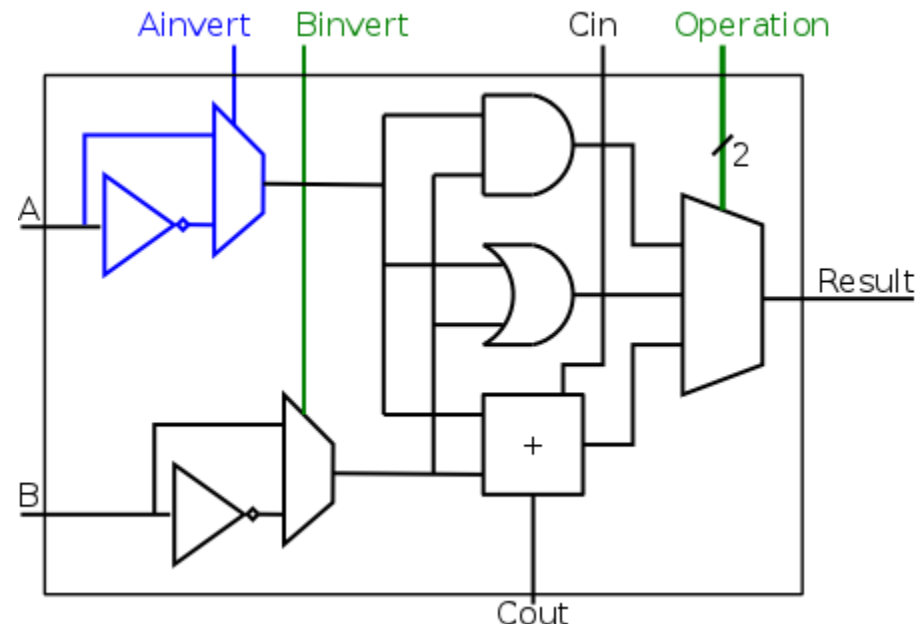
## 5. One Bit At A Time

**Note:** We will revisit this when we cover combinational circuits later.


- A simplified 1-bit MIPS ALU can be implemented as follows:
- 4 control bits are needed:
  - **Ainvert:**
    - 1 to invert input A
  - **Binvert:**
    - 1 to invert input B
  - **Operation** (2-bit)
    - To select one of the 3 results



## 5. One Bit At A Time (Aha!)

- Can you see how the **ALUcontrol** (4-bit) signal controls the ALU?
  - Note: implementation for **slt** not shown

ALUcontrol			Function
Ainvert	Binvert	Operation	
0	0	00	AND
0	0	01	OR
0	0	10	add
0	1	10	subtract
0	1	11	slt
1	1	00	NOR

 

## 5. Multilevel Decoding

- Now we can start to design for **ALUcontrol** signal, which depends on:
  - Opcode (6-bit) field **and** Function Code (6-bit) field
- **Brute Force approach:**
  - Use Opcode and Function Code directly, i.e. finding expressions with 12 variables
- **Multilevel Decoding approach:**
  - Use some of the input to reduce the cases, then generate the full output
  - Simplify the design process, reduce the size of the main controller, potentially speedup the circuit



## 5. Intermediate Signal: **ALUop**

### ■ Basic Idea:


1. Use Opcode to generate a 2-bit **ALUop** signal
  - Represents classification of the instructions:

Instruction type	<b>ALUop</b>
lw / sw	00
beq	01
R-type	10

2. Use **ALUop** signal and Function Code field (for R-type instructions) to generate the 4-bit **ALUcontrol** signal



# 5. Two-level Implementation

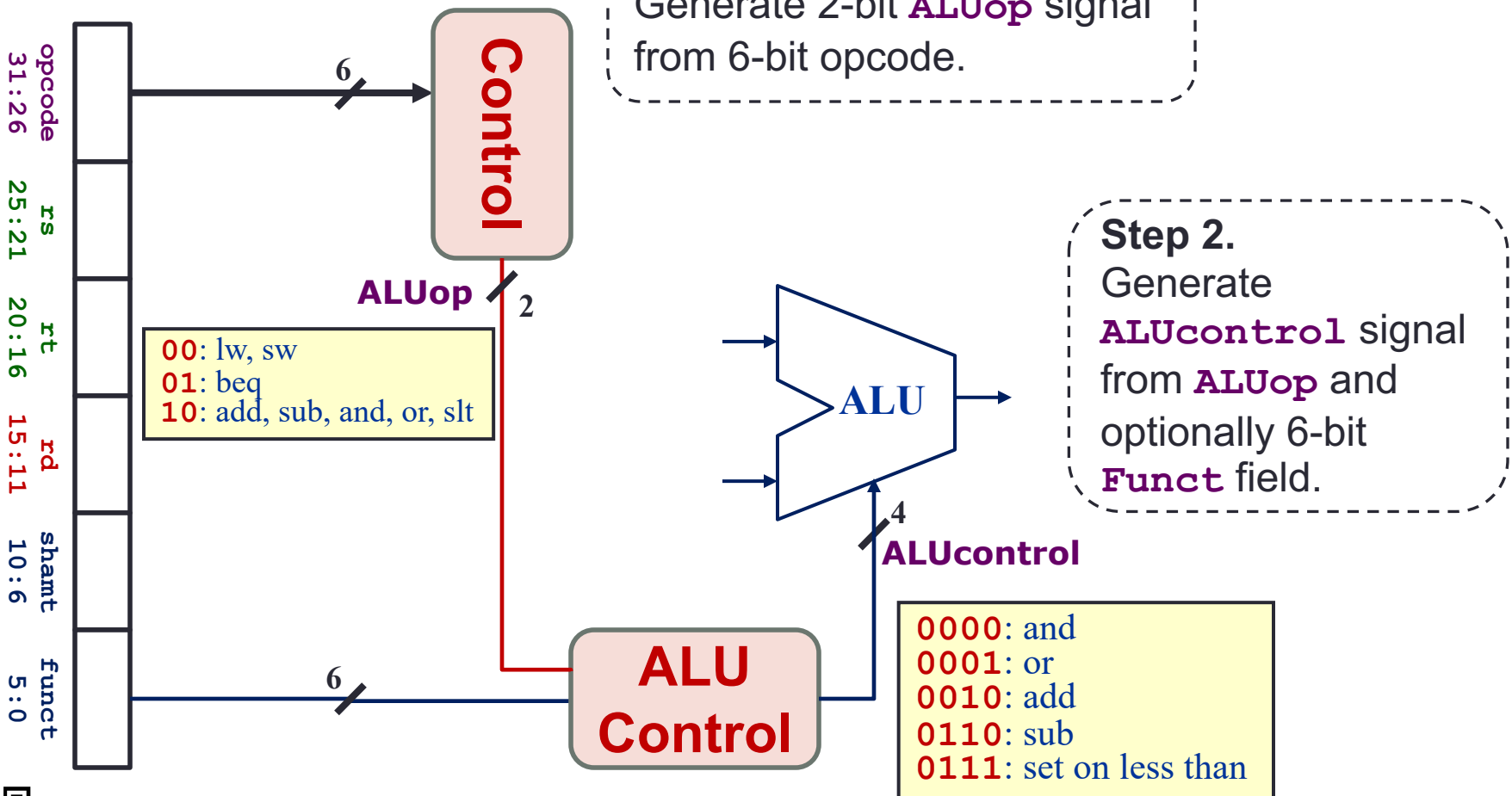



# 5. Generating ALUcontrol Signal

Opcode	ALUop	Instruction Operation	Funct field	ALU action	ALU control
lw		load word		add	
sw		store word		add	
beq		branch equal		subtract	
R-type		add		add	
R-type		subtract		subtract	
R-type		AND		AND	
R-type		OR		OR	
R-type		set on less than		set on less than	

Instruction Type	ALUop
lw / sw	00
beq	01
R-type	10

ALUcontrol	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	slt
1100	NOR

Generation of 2-bit **ALUop** signal will be discussed later



## 5. Design of ALU Control Unit (1/2)

- **Input:** 6-bit **Funct** field and 2-bit **ALUop**
- **Output:** 4-bit **ALUcontrol**
- Find the simplified expressions

ALUcontrol3 = 0

ALUcontrol2 = ?


$\text{ALUop0} + \text{ALUop1} \cdot \text{F1}$

	ALUop		Funct Field ( F[5:0] == Inst[5:0] )						ALU control
	MSB	LSB	F5	F4	F3	F2	F1	F0	
lw									
sw									
beq									
add									
sub									
and									
or									
slt									
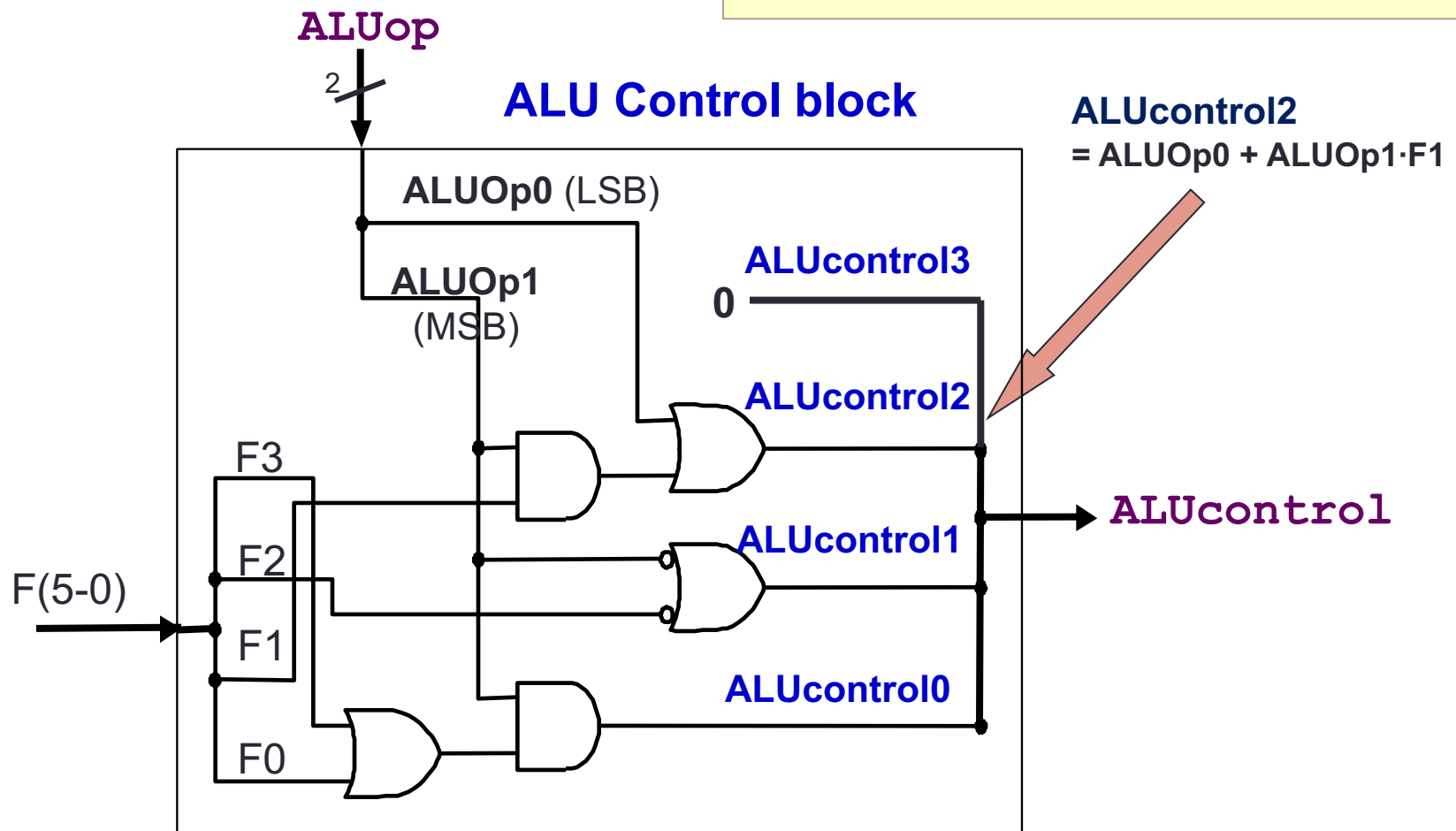
## 5. Design of ALU Control Unit (2/2)

- Simple combinational logic


**Note:** We will revisit this when we cover combinational circuits later.


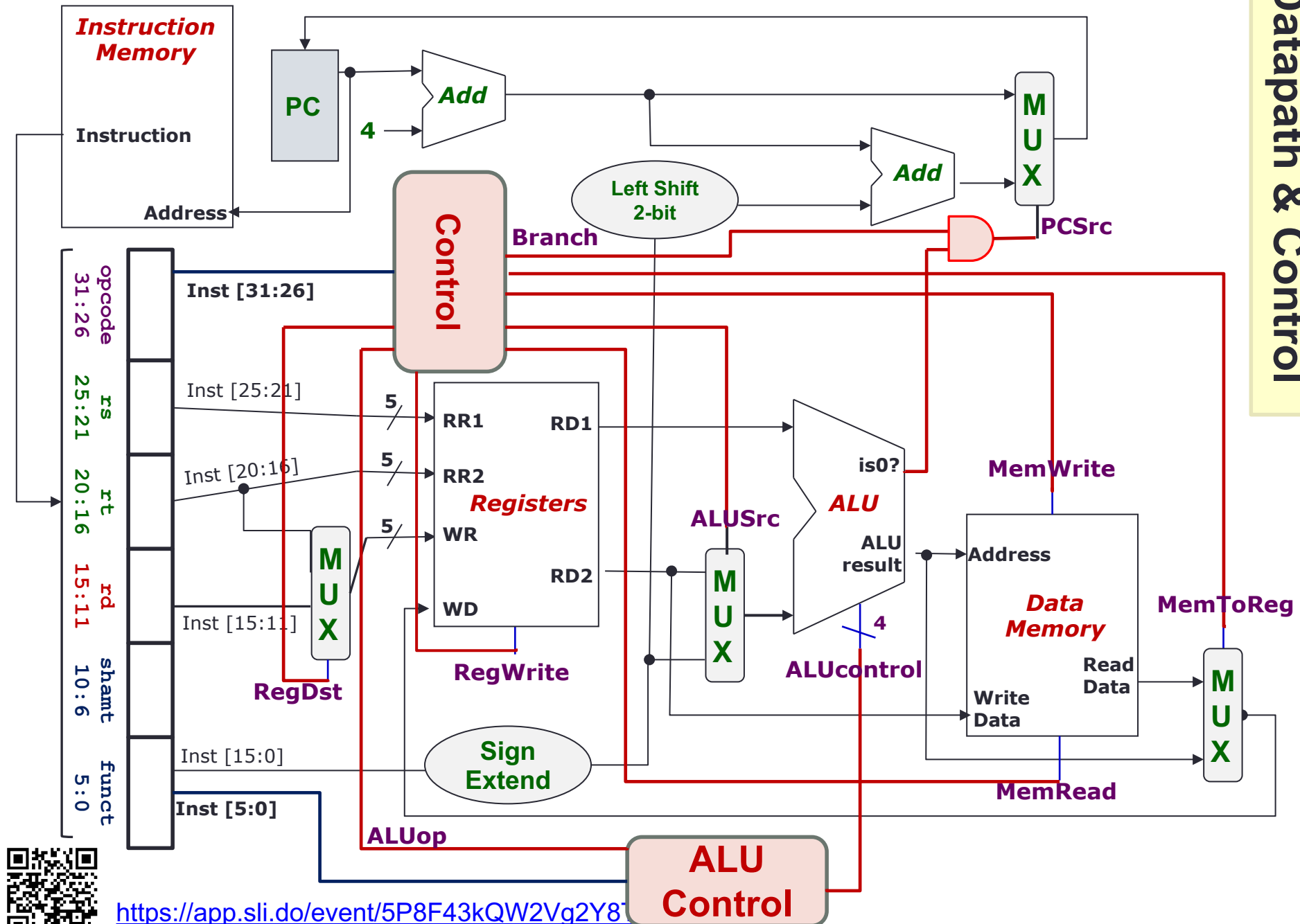
## 5. Finale: Control Design


- We have now considered all individual signals and their expected values
  - ➔ Ready to design the controller itself
- Typical digital design steps:
  - Fill in truth table
    - **Input:** Opcode
    - **Output:** Various control signals as discussed
  - Derive simplified expression for each signal





## 5. Control Design: Outputs

	RegDst	ALUSrc	MemToReg	RegWrite	MemRead	MemWrite	Branch	ALUOp	
								op1	op0
R-type	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

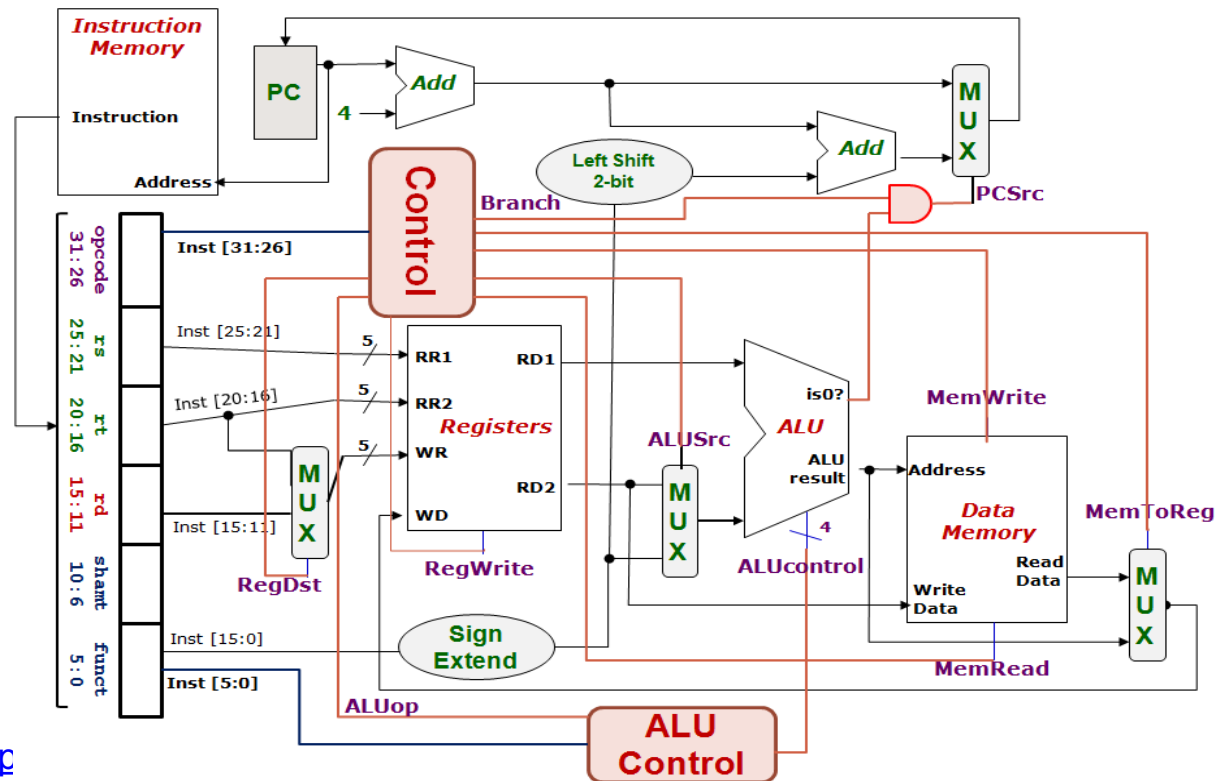


## 5. Control Design: Inputs

	Opcode ( Op[5:0] == Inst[31:26] )						
	Op5	Op4	Op3	Op2	Op1	Op0	Value in Hexadecimal
<b>R-type</b>	0	0	0	0	0	0	0
<b>lw</b>	1	0	0	0	1	1	23
<b>sw</b>	1	0	1	0	1	1	2B
<b>beq</b>	0	0	0	1	0	0	4

- With the input (opcode) and output (control signals), let's design the circuit



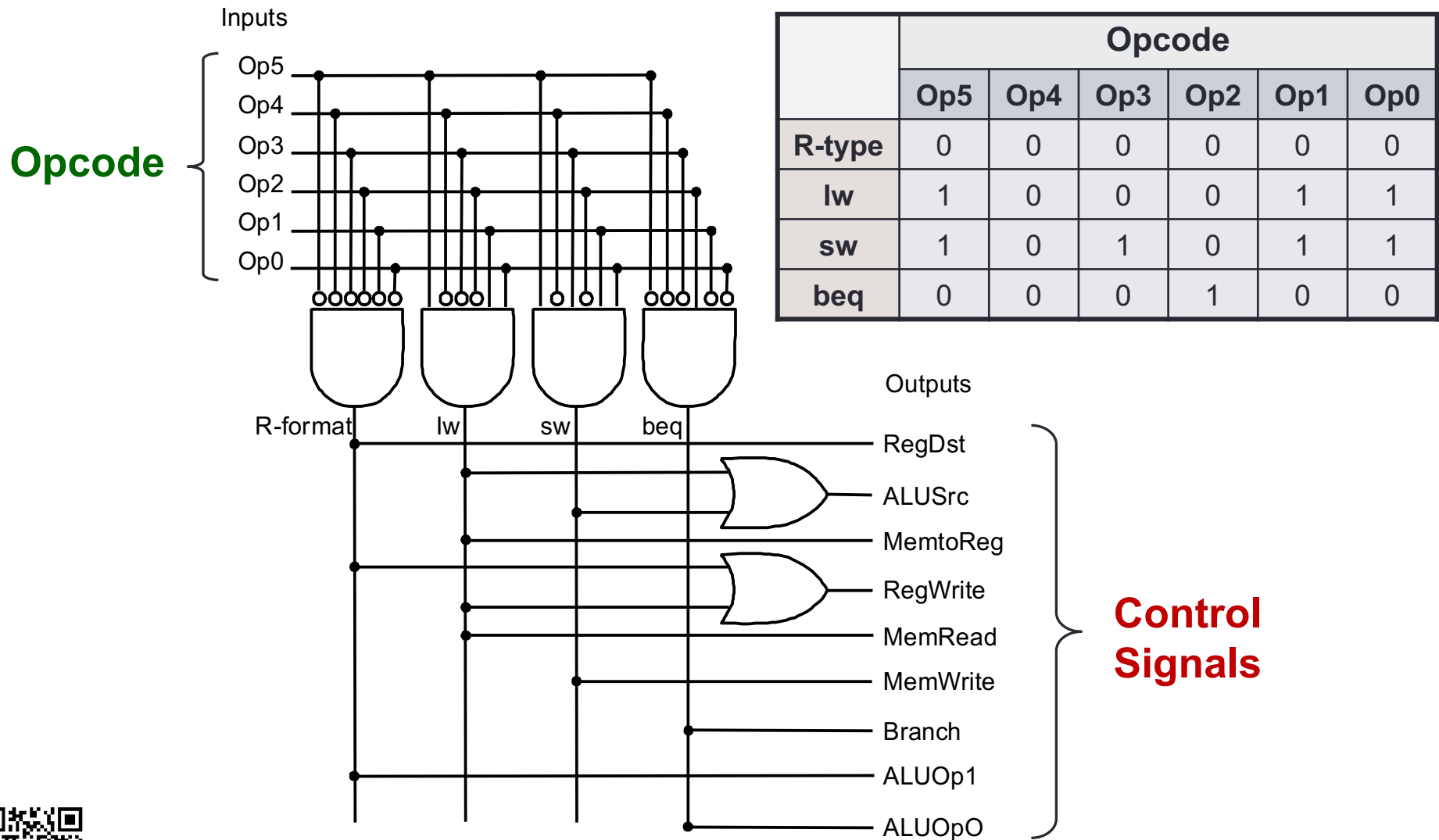
# 5. Combinational Circuit Implementation





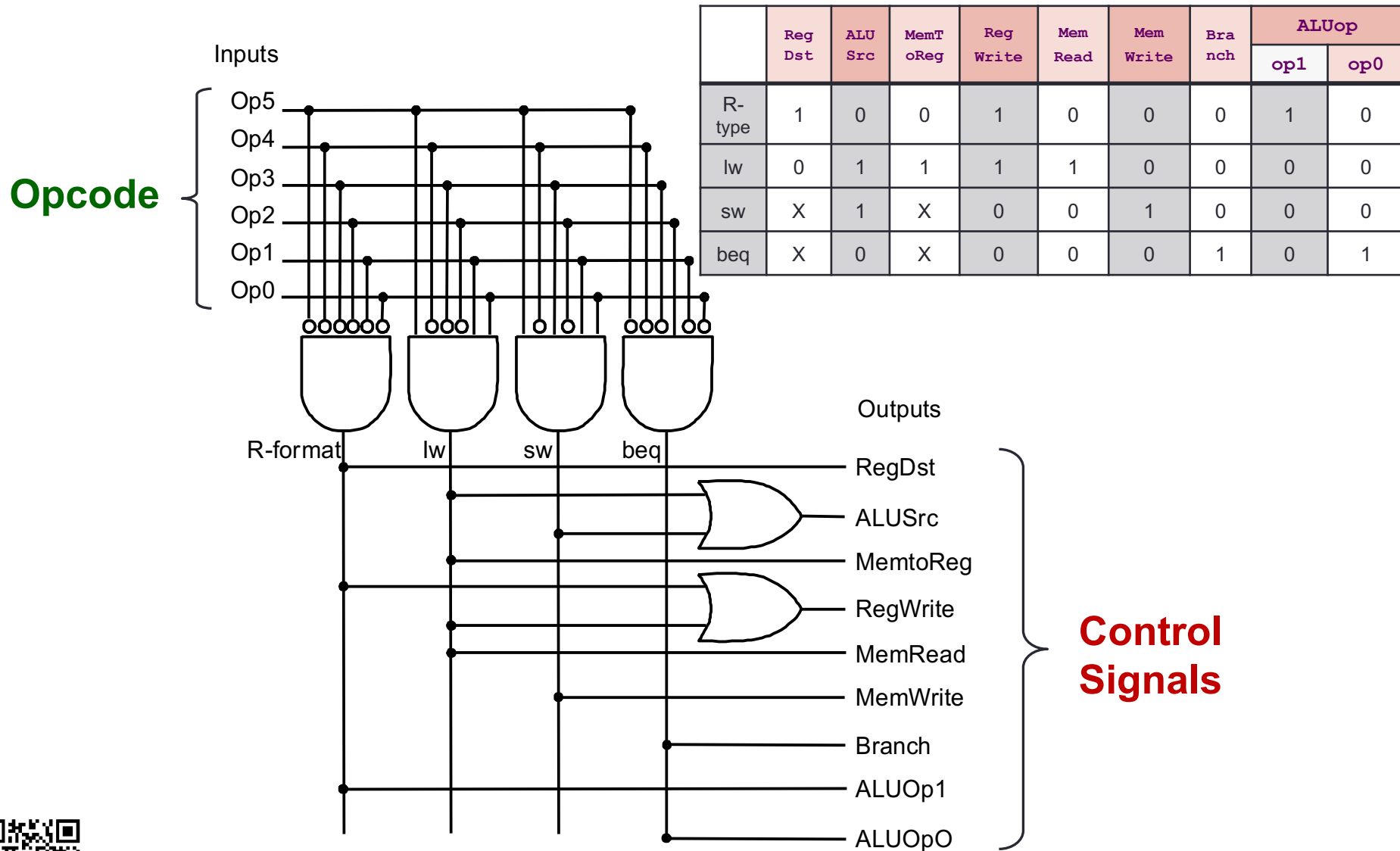
# 5. Combinational Circuit Implementation


 
## 6. Big Picture: Instruction Execution

- Instruction Execution =
  1. Read contents of one or more storage elements (register/memory)
  2. Perform computation through some combinational logic
  3. Write results to one or more storage elements (register/memory)
- All these performed **within a clock period**



Don't want to read a storage element when it is being written.



## 6. Single Cycle Implementation: Shortcoming

- Calculate cycle time assuming negligible delays: memory (2ns), ALU/adders (2ns), register file access (1ns)

Instruction	Inst Mem	Reg read	ALU	Data Mem	Reg write	Total
ALU	2	1	2		1	6
lw	2	1	2	2	1	8
sw	2	1	2	2		7
beq	2	1	2			5

- All instructions take as much time as the slowest one (i.e., load)
  - Long cycle time for each instruction



## 6. Solution #1: Multicycle Implementation

- Break up the instructions into execution steps:
  1. Instruction fetch
  2. Instruction decode and register read
  3. ALU operation
  4. Memory read/write
  5. Register write
- Each execution step **takes one clock cycle**
  - ➔ **Cycle time is much shorter, i.e., clock frequency is much higher**
- Instructions take variable number of clock cycles to complete execution
- Not covered in class:
  - See Section 5.5 of COD if interested



## 6. Solution #2: Pipelining

- Break up the instructions into execution steps one per clock cycle
- Allow different instructions to be in different execution steps simultaneously
- Covered in a later lecture



# Summary

- A very simple implementation of MIPS datapath and control for a subset of its instructions
- Concepts:
  - An instruction executes in a single clock cycle
  - Read storage elements, compute, write to storage elements
  - Datapath is shared among different instructions types using MUXs and control signals
  - Control signals are generated from the machine language encoding of instructions



# Reading

- **The Processor: Datapath and Control**
  - COD Chapter 5 Sections 5.4 (3<sup>rd</sup> edition)
  - COD Chapter 4 Sections 4.4 (4<sup>th</sup> edition)
- **Exploration:**
  - ALU design and implementation:
    - 4<sup>th</sup> edition (MIPS): Appendix C
    - <http://cs.nyu.edu/courses/fall11/CSCI-UA.0436-001/class-notes.html>



<https://app.sli.do/event/5P8F43kQW2Vg2Y8TTRVzHu>

# End of File



<https://app.sli.do/event/5P8F43kQW2Vg2Y8TTRVzHu>