

CS2100

COMPUTER ORGANISATION

<http://www.comp.nus.edu.sg/~cs2100/>

## Lecture #19

---

# Sequential Logic



**NUS**  
National University  
of Singapore

School of  
Computing

<https://app.sli.do/event/aanrHmK6Geu3scZbeLh6wx>



# Lecture #19: Sequential Logic (1/2)

1. Introduction
2. Memory Elements
3. Latches
  - 3.1 *S-R* Latch
  - 3.2 *D* Latch
4. Flip-flops
  - 4.1 *S-R* Flip-flop
  - 4.2 *D* Flip-flop
  - 4.3 *J-K* Flip-flop
  - 4.4 *T* Flip-flop



# Lecture #19: Sequential Logic (2/2)

## 5. Asynchronous Inputs

## 6. Synchronous Sequential Circuit

### 6.1 Flip-flop Characteristic Tables

### 6.2 Analysis

### 6.3 Flip-flop Excitation Tables

### 6.4 Design

## 7. Memory

### 7.1 Memory Unit

### 7.2 Read/Write Operations

### 7.3 Memory Cell

### 7.4 Memory Arrays




# 1. Introduction (1/2)

- Two classes of logic circuits
  - Combinational
  - Sequential


- **Combinational Circuit**

 - Each output depends entirely on the immediate (present) inputs.



- **Sequential Circuit**

 - Each output depends on both present inputs and state.




# 1. Introduction (2/2)

- Two types of sequential circuits:
  - **Synchronous**: outputs change only at specific time
  - **Asynchronous**: outputs change at any time
- Multivibrator: a class of sequential circuits
  - Bistable (2 stable states)
  - Monostable or one-shot (1 stable state)
  - Astable (no stable state)
- Bistable logic devices
  - **Latches** and **flip-flops**.
  - They differ in the methods used for changing their state.


 
## 2. Memory Elements (1/3)

- **Memory element:** a device which can remember value indefinitely, or change value on command from its inputs.



- **Characteristic table:**

Command (at time $t$ )	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1


$Q(t)$  or  $Q$ : current state

$Q(t+1)$  or  $Q^+$ : next state




## 2. Memory Elements (2/3)

- Memory element with clock.

 

- Clock** is usually a square wave.

 

## 2. Memory Elements (3/3)

- Two types of triggering/activation


- Pulse-triggered
- Edge-triggered

- Pulse-triggered

- Latches
- ON = 1, OFF = 0

- Edge-triggered

 - Flip-flops
- Positive edge-triggered (ON = from 0 to 1; OFF = other time)
- Negative edge-triggered (ON = from 1 to 0; OFF = other time)






## 3.1 S-R Latch (1/3)

- Two inputs:  $S$  and  $R$ .
- Two complementary outputs:  $Q$  and  $Q'$ .
  - When  $Q = \text{HIGH}$ , we say latch is in **SET** state.
  - When  $Q = \text{LOW}$ , we say latch is in **RESET** state.
- For active-high input S-R latch (also known as NOR gate latch)
  - $R = \text{HIGH}$  and  $S = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
  - $S = \text{HIGH}$  and  $R = \text{LOW} \rightarrow Q$  becomes HIGH (SET state)
  - Both  $R$  and  $S$  are LOW  $\rightarrow$  No change in output  $Q$
  - Both  $R$  and  $S$  are HIGH  $\rightarrow$  Outputs  $Q$  and  $Q'$  are both LOW (invalid!)
- Drawback: invalid condition exists and must be avoided.




## 3.1 S-R Latch (2/3)

- Active-high input S-R latch:

 


- Block diagram:

 
 
## 3.1 S-R Latch (3/3)

- **Characteristic table** for active-high input S-R latch:



S	R	Q	Q'	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

S	R	Q(t+1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	indeterminate	



$$Q(t+1) = S + R' \cdot Q$$

$$S \cdot R = 0$$


  
## 3.1 Active-Low S-R Latch

- (You may skip this slide.)
- What we have seen is **active-high input S-R** latch.
- There are **active-low input S-R** latches, where NAND gates are used instead. See diagram on the left below.




- In this case,
  - when  $R=0$  and  $S=1$ , the latch is reset (i.e.  $Q$  becomes 0)
  - when  $R=1$  and  $S=0$ , the latch is set (i.e.  $Q$  becomes 1)
  - when  $S=R=1$ , it is a no-change command.
  - when  $S=R=0$ , it is an invalid command.
- Sometimes, we use the alternative gate diagram for the NAND gate. See diagram on the right above. (This appears in more complex latches/flip-flops in the later slides.)

(Sometimes, the inputs are labelled as  $S'$  and  $R'$ .)


 
## 3.1 Gated S-R Latch

- S-R latch + *enable input* ( $EN$ ) and 2 NAND gates → a **gated S-R latch**.





- Outputs change (if necessary) only when  $EN$  is high.


  
## 3.2 Gated $D$ Latch (1/2)

- Make input  $R$  equal to  $S'$   $\rightarrow$  gated  $D$  latch.
- $D$  latch eliminates the undesirable condition of invalid state in the  $S$ - $R$  latch.



## 3.2 Gated $D$ Latch (2/2)

- When  $EN$  is high,
  - $D = \text{HIGH} \rightarrow$  latch is SET
  - $D = \text{LOW} \rightarrow$  latch is RESET
- Hence when  $EN$  is high,  $Q$  “follows” the  $D$  (data) input.
- **Characteristic table:**


$EN$	$D$	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change

When  $EN=1$ ,  $Q(t+1) = D$


 
## 4. Flip-flops (1/2)


- Flip-flops are synchronous bistable devices.
- Output changes state at a specified point on a triggering input called the **clock**.
- Change state either at the positive (rising) edge, or at the negative (falling) edge of the clock signal.





 
## 4. Flip-flops (2/2)

- *S-R* flip-flop, *D* flip-flop, and *J-K* flip-flop.
- Note the “>” symbol at the clock input.



Positive edge-triggered flip-flops

 


Negative edge-triggered flip-flops


 
## 4.1 S-R Flip-flop

- **S-R flip-flop**: On the triggering edge of the clock pulse,
  - $R = \text{HIGH}$  and  $S = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
  - $S = \text{HIGH}$  and  $R = \text{LOW} \rightarrow Q$  becomes HIGH (SET state)
  - Both  $R$  and  $S$  are LOW  $\rightarrow$  No change in output  $Q$
  - Both  $R$  and  $S$  are HIGH  $\rightarrow$  Invalid!
- **Characteristic table** of positive edge-triggered S-R flip-flop:



S	R	CLK	$Q(t+1)$	Comments
0	0	X	$Q(t)$	No change
0	1	$\uparrow$	0	Reset
1	0	$\uparrow$	1	Set
1	1	$\uparrow$	?	Invalid


X = irrelevant ("don't care")

$\uparrow$  = clock transition LOW to HIGH


 
## 4.2 *D* Flip-flop (1/2)

- ***D* flip-flop**: Single input *D* (data). On the triggering edge of the clock pulse,
  - $D = \text{HIGH} \rightarrow Q$  becomes HIGH (SET state)
  - $D = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
- Hence, *Q* “follows” *D* at the clock edge.
- Convert *S-R* flip-flop into a *D* flip-flop: add an inverter.



A positive edge-triggered *D* flip-flop formed with an *S-R* flip-flop.


<i>D</i>	<i>CLK</i>	<i>Q</i> ( <i>t</i> +1)	Comments
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH


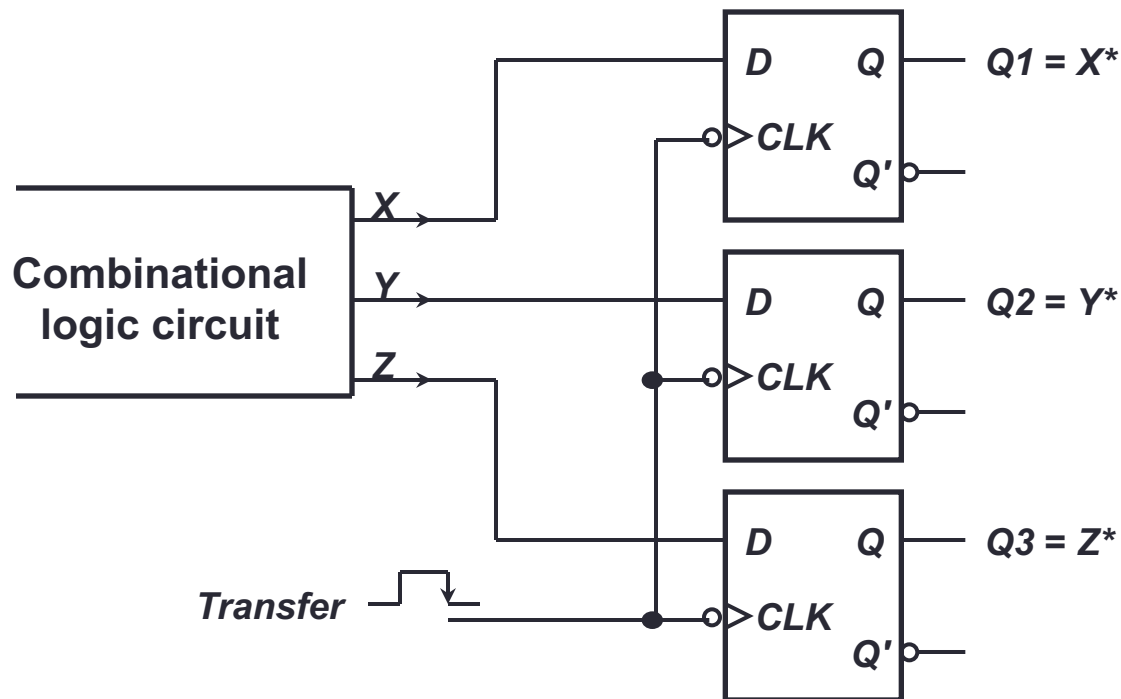
## 4.2 D Flip-flop (2/2)

- Application: Parallel data transfer.
  - To transfer logic-circuit outputs  $X$ ,  $Y$ ,  $Z$  to flip-flops  $Q1$ ,  $Q2$  and  $Q3$  for storage.



\* After occurrence of negative-going transition




## 4.3 *J-K* Flip-flop (1/2)

- *J-K* flip-flop:  $Q$  and  $Q'$  are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a toggle state
  - $J = \text{HIGH}$  and  $K = \text{LOW} \rightarrow Q$  becomes HIGH (SET state)
  - $K = \text{HIGH}$  and  $J = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
  - Both  $J$  and  $K$  are LOW  $\rightarrow$  No change in output  $Q$
  - Both  $J$  and  $K$  are HIGH  $\rightarrow$  Toggle



## 4.3 J-K Flip-flop (2/2)

- $J$ - $K$  flip-flop circuit:

 

- Characteristic table:

$J$	$K$	$CLK$	$Q(t+1)$	Comments
0	0	$\uparrow$	$Q(t)$	No change
0	1	$\uparrow$	0	Reset
1	0	$\uparrow$	1	Set
1	1	$\uparrow$	$Q(t)'$	Toggle


$$Q(t+1) = J \cdot Q' + K' \cdot Q$$

$Q$	$J$	$K$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


 
## 4.4 T Flip-flop

- **T flip-flop**: Single input version of the *J-K* flip-flop, formed by tying both inputs together.



- **Characteristic table:**

$T$	$CLK$	$Q(t+1)$	Comments
0	↑	$Q(t)$	No change
1	↑	$Q(t)'$	Toggle

$Q$	$T$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = T \cdot Q' + T' \cdot Q$$



## 5. Asynchronous Inputs (1/2)



- $S$ - $R$ ,  $D$  and  $J$ - $K$  inputs are **synchronous inputs**, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock; example: *preset* ( $PRE$ ) and *clear* ( $CLR$ ) [or *direct set* ( $SD$ ) and *direct reset* ( $RD$ )].
- When  $PRE$ =HIGH,  $Q$  is immediately set to HIGH.
- When  $CLR$ =HIGH,  $Q$  is immediately cleared to LOW.
- Flip-flop in normal operation mode when both  $PRE$  and  $CLR$  are LOW.




  
## 5. Asynchronous Inputs (2/2)

- A  $J$ - $K$  flip-flop with active-low PRESET and CLEAR asynchronous inputs.



# End of File

